

Exam. Code : 103205

Subject Code : 1412

B.A./B.Sc. 5th Semester

PHYSICS (Electronics)

Paper-B

Time Allowed—3 Hours]

[Maximum Marks—35

Note : Section A is compulsory. Attempt **one** question from Sections B, C, D and E.

SECTION-A

1. (a) What is the difference between an ideal voltage source and practical voltage source ?
- (b) What is the charge on a *p*-type or *n*-type semiconductor ?
- (c) Describe the filtering action of a capacitor.
- (d) Why the base of a transistor is made very thin as compared to that of emitter and collector ?
- (e) Calculate the gain of a negative feedback amplifier with an internal gain, $A = 100$ and feedback factor,
$$\beta = \frac{1}{10}.$$
- (f) Why at least three RC sections are used in Phase shift oscillator ?
- (g) What is the power dissipation in the Zener diode ?

$$7 \times 1 = 7$$

SECTION-B

2. Discuss the difference between the centre tapped and bridge type Full Wave Rectifier (FWR). Show that the Peak Inverse Voltage (PIV) becomes half in a bridge rectifier in comparison to a centre tapped rectifier. 7
3. Discuss and draw the I-V characteristics of a p-n diode and show that total current through it is given by the expression $I = \left[\exp\left(\frac{eV}{kT}\right) - 1 \right]$, where symbols have their usual meanings. 7

SECTION-C

4. Define stability factor. Draw a fixed bias circuit diagram and derive an expression for its stability factor. Also give advantages of this technique. 7
5. Explain the terms saturation voltage and saturation current in connection with a common source drain characteristics. How do they vary when gate reverse bias increases ? 7

SECTION-D

6. Draw the low frequency h-parameters equivalent circuit of a CE transistor amplifier. Derive expressions for input resistance, output resistance, current gain, voltage gain and power gain. 7

7. Show that negative feedback (a) reduces the phase distortion of an amplifier and (b) improves the gain stability and reduces the noise level of an amplifier. 7

SECTION-E

8. Describe the operation of a tuned collector oscillator from the circuit diagram. Derive the condition from the sustained oscillations. 7
9. Draw the circuit diagram of a phase shift oscillator and explain its working. 7