

Exam. Code : 103205

Subject Code : 1363

B.A./B.Sc. 5th Semester

PHYSICS

Paper-B (Electronics)

Time Allowed—3 Hours]

[Maximum Marks—35

**Note** :—Section A is compulsory. Attempt **ONE** question from Sections B, C, D and E. All questions carries equal marks.

## SECTION—A

1. (a) Why a semiconductor behaves like an insulator at 0K ?
- (b) Explain the formation of depletion region in a  $p-n$  junction.
- (c) Why is silicon not suitable for the design of LED ?
- (d) What are the differences between the emitter and collector regions of a transistor ?
- (e) Obtain the relation between transistor  $\alpha$  and  $\beta$ .
- (f) BJT is a current controlled device but JFET is a voltage controlled device. Comment.
- (g) Draw the block diagram of a feedback amplifier. State the function of each block.

**SECTION—B**

2. Explain the working of  $L$  section filter with full wave rectifier (FWR). Show that the ripple factor is independent of load resistance.
3. Discuss and draw the  $I-V$  characteristics of a  $p-n$  junction and also obtain expression for its static and dynamic resistance from the diode equation.

**SECTION—C**

4. Draw circuit diagram of a  $p-n-p$  transistor in  $CE$  mode for drawing output characteristic curves. Explain how the two constants of the transistor can be obtained from these curves.
5. Draw the characteristics of an n-channel JFET. What is pinch off voltage ?

**SECTION—D**

6. Explain the working principle of a feedback amplifier. Find the expression for the voltage gain with feedback.
7. Discuss  $h$  parameters for a transistor. Using two hybrid parameter equations draw the equivalent circuit for transistor in a  $CE$  mode.

**SECTION—E**

8. With a suitable circuit diagram, explain the operation of a phase shift oscillator. Find the expressions for frequency of oscillation and condition of oscillation.
9. Draw the circuit diagram of a Hartley oscillator and explain its action. Obtain the frequency and condition of oscillation of this oscillator.