

2316

95

Class - BCA/B.Sc.(IT) 2nd Sem.

Subject - Principles of Digital Electronics

Paper - II (BCA), III (B.Sc. IT)

Time Allowed : 3 Hours

Maximum Marks : 75

Note:- Non- Programmable and Non-storage type calculator is allowed.

Attempt any 5 questions.

1. Perform the following :-

- (a) $(1AF)_{16}$ to $()_8$ 5
- (b) $(521.63)_8 \rightarrow (?)_{10}$ 5
- (c) Subtract $(3)_{10}$ from $(4)_{10}$ using 2's complement 2
- (d) Construct the truth table for $z = xy + \bar{x} \bar{y}$ 3

2. Write a Note on :-

- (i) De - Morgan's Law 5
- (ii) Duality Theorem 5
- (iii) Importance of K-Map 5

3. Minimize the following Boolean Expression and also design circuit for each

(i) $Y = \overline{ABCD} + \overline{ABCD} ABCD + ABC\bar{D} + \overline{ABC} + \overline{ABC}$

(ii) $Y = \bar{A}B + \bar{B}C + \bar{C}D + \bar{D}A + AB + BC + CD + DA$

(iii) Explain 2 : 4 Line Decoder 3x5=15

1

4. Explain -
- Priority Encoder
 - Convert $F(A,B,C) = (A' + B)(B' + C)$ in product of maxterms.
 - Find canonical SOP form of $F = AB + BC + \bar{A}$ 3x5=15
5. Explain Minterms and Maxterms. Minimize the following using K-Map and also draw the circuit
- $F(A,B,C,D) = \pi M(2, 3, 8, 9, 12, 13, 15)$
 - $F = \sum m(0, 1, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11)$
 - $Y(A, B, C) = \sum m(0, 2, 3, 4) + d(6)$ 3x5=15
6. What do you mean by combinational circuits? Implement Full Adder using two Half Adders. Write down the truth table of a Full Adder. 15
7. What do you mean by Multiplexer? Design 16:1 Mux using 4:1 Mux. Also show its truth table. 15
8. What do you mean by Universal Gates? Explain how NAND is a Universal Gate. 15
