

Exam. Code : 107202

Subject Code : 2044

BCA Semester—II

PRINCIPLES OF DIGITAL ELECTRONICS

Paper—II

Time Allowed—3 Hours]

[Maximum Marks—75

Note : Attempt any FIVE questions.

1. (a) Show that NAND gates are universal gates. 7.5
(b) Using 2's complement notation perform the following arithmetic operations using 8 bit register(s) :
 - (i) $25 + (-12)$ (ii) $17 - 6$
 - (iii) $-18 - 16$ (iv) $18 + (18)$
 - (v) $12 - (-19)$ 7.5
2. (a) Discuss in brief De Morgan's theorems with example.
(b) Write a short note on don't care conditions.
(c) Simplify the expression :
$$AB + A(B + C) + B(B + C).$$
 5×3
3. (a) Explain SOP form and POS form of logic expression.
(b) What is meant by the base of a number system ? Give examples to illustrate the role of base in positional number system.
(c) Distinguish between combinational and sequential circuits. 5×3

3082(2517)/STB-14035

(Contd.)

4. Write the truth table of a Full Adder and then from it derive the circuit in terms of half adders. 15
5. Draw the circuit of an S-R Flip Flop using NAND gates only. From it derive the circuit of a D-Flip Flop and explain its truth table. 10
- Draw the circuit of a 2 to 4 decoder and explain its function. 5
6. (a) What are counters ? Explain the working of a typical counter in detail. 10
- (b) Distinguish between static and dynamic devices. 5
7. (a) Explain the working of a RAM cell. 10
- (b) Explain the read and write memory operations in detail. 5
8. (a) Explain various types of memory and their characteristics. 10
- (b) Explain the address selection logic in PROMS. 5