

Bachelor of Computer Application (BCA) 2nd Semester**PRINCIPLES OF DIGITAL ELECTRONICS****Paper—II**

Time Allowed—Three Hours] [Maximum Marks—75

Note :— Attempt FIVE questions in all.

1. (a) Perform the following additions using 2s complement :

(i) -20 to $+26$

(ii) 25 to -15 7.5

- (b) Using 2's complement notation perform the following arithmetic operations using 8 bit register(s) :

(i) $25 + (-12)$

(ii) $17 - 6$

(iii) $-18 - 16$

(iv) $-8 + (18)$

(v) $12 - (-19)$ 7.5

2. (i) Convert the decimal number 430 to Excess-3 code. 7.5

- (ii) Convert the binary number 10110 to Gray code. 7.5

3. (a) Simplify $y = (A + B)(A + B')(A' + B')$ by using laws and theorems of Boolean Algebra. 7.5
- (b) Explain the various laws of Boolean algebra. 7.5
4. Solve the following using K-map :
- $$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 7, 12, 13, 14) + \Sigma d(1, 4, 11, 15)$$
- Here d denotes the don't care condition. 15
5. (a) Describe the need of a multiplexer in a system. How is a multiplexer different from a decoder ? Draw the logic diagram of 8×1 multiplexer and 2×4 decoder. 7.5
- (b) Explain the working of a S-R flip-flop using its logic diagram and truth-table. 7.5
6. (a) Explain the working of a full subtractor in detail. 7.5
- (b) Write the truth table of J-K flip-flop and explain how race-around problem can be solved in it. 7.5
7. (a) Distinguish between static and dynamic devices. 7.5
- (b) Explain the RAM memory read operation. 7.5
8. (a) Explain the EPROM address selection Logic. 7.5
- (b) What is a counter ? Explain the working of a counter with the help of the truth table and timing diagram. 7.5