

Exam. Code : 107202

Subject Code : 1734

Bachelor of Computer Application (BCA) 2nd Semester

PRINCIPLES OF DIGITAL ELECTRONICS

Paper—II

Time Allowed—Three Hours] [Maximum Marks—75

Note :— Attempt **FIVE** questions in all, selecting at least **ONE** question from each section.

SECTION—A

1. Perform the following number conversions :—

(i) $(3FEF)_{16} = (?)_{10}$

(ii) $(F432)_{16} = (?)_2$

(iii) $(65)_8 = (?)_2$

(iv) $(56)_{10} = (?)_2$

(v) $(B3D8)_{16} = (?)_8$

(vi) $(1011.101)_2 = (?)_{16}$

(vii) $(AB.CD)_{16} = (?)_{10}$

(viii) $(72.22)_8 = (?)_{16}$

15

2. Using 2's complement notation perform the following arithmetic operations using 8 bit register(s) :

(i) $25 + (-12)$

(ii) $17 - 6$

(iii) $-18 - 16$

(iv) $-8 + (18)$

(v) $12 - (-19)$.

15

SECTION—B

3. Verify the following gate with truth table :

(i) AND

(ii) OR

(iii) NOT

(iv) NAND

(v) NOR

(vi) XOR

(vii) XNOR.

15

4. Simplify F together with don't care conditions d in
(i) SOP (ii) POS form :

$$F(w, x, y, z) = \Sigma(1, 2, 8, 9, 12, 13),$$

$$d(w, x, y, z) = \Sigma(10, 11, 14, 15).$$

15

SECTION—C

5. (a) Design a 3 : 8 decoder using basic gates. 7.5
(b) Explain the function of a full adder with a truth table, logic circuit and block diagram. 7.5

6. (a) Explain the functioning of Multiplexer and Demultiplexer in detail. 7.5
- (b) Draw the circuit of an S-R Flip Flop using NAND gates only. From it derive the circuit of a D-Flip Flop and explain its truth table. 7.5

SECTION—D

7. (a) Compare static RAMs and dynamic RAMs. 7.5
- (b) Discuss the classification of ROM and RAM memories. 7.5
8. (a) Explain read and write operation of memory with timing waveforms. 7.5
- (b) Explain PROM and EPROM address selection logic. 7.5