

Exam. Code : 105702

Subject Code : 1561

**B.Sc. (Information Technology) 2<sup>nd</sup> Semester**  
**PRINCIPLES OF DIGITAL ELECTRONICS**

**Paper—III**

Time Allowed—Three Hours] [Maximum Marks—75

**Note** :— Attempt any **FIVE** questions. All questions carry equal marks.

1. Describe Gray code and BCD code. Convert  $(35.12)_8$  into binary.
2. Design a Modulo-10 counter and explain its working.
3. Design a full adder using NAND gates only.
4. (i) Convert  $AC + AB + BC + BD$  to POS form.  
(ii) Simplify  $F = \Sigma(1, 2, 4, 6, 8)$  using Boolean algebra.
5. Explain the working of JK flip-flop.
6. Write a note on PROMs. How is address selection logic used to select a device out of a number of devices connected ?
7. Write the steps of K-map simplification and simplify  $\Sigma(1, 2, 4, 6, 8, 11, 13, 14)$  using K-map.
8. (i) Differentiate PROM, EPROM and ROM.  
(ii) Excess 3 code.