# a2zpapers.com

Exam. Code : 105702 Subject Code : 1424

# B.Sc. (Information Technology) 2<sup>nd</sup> Semester PRINCIPLES OF DIGITAL ELECTRONICS Paper—I

Time Allowed—3 Hours] [Maximum Marks—75 Note :— Attempt *five* questions in all selecting at least *one* question from each section. All questions carry equal marks.

## SECTION-A

- 1. (i) Describe Gray code. Convert 7AC into Octal.
  - (ii) Convert the following :
    - (a) Convert (26.3), into binary
    - (b) Convert 11010110010 into BCD.

## 2. Do the following :

- (i) Find 1's and 2's complement of 27.
- (ii) Write the excess-three codes for decimal numbers 5 and 219.

## SECTION-B

- 3. (i) Simplify  $F = \Sigma(1, 2, 4, 6, 8)$  using Boolean algebra.
  - (ii) Write the steps of K-map simplification and simplify  $\Sigma(1, 2, 4, 6, 8, 11, 13, 14)$  using K-map.
- 4. (i) Simplify  $F = \Sigma(1, 2, 4, 6, 13)$  using Boolean algebra and design the circuit using NAND gates only.

1

(ii) Convert  $(A+\overline{B}+C)(\overline{A}+B)(B+C)$  into SOP form.

#### 3051(2519)/EBH-1131

### (Contd.)

www.a2zpapers.com www.a2zpapers.com

ad free old Question papers gndu, ptu hp board, punjak

## SECTION-C

- 5. (i) Explain the working of master-slave flip-flop.
  - (ii) Explain the working of serial in serial out shift register.
- 6. (i) Design and explain the working of a 1 to 4 de-multiplexer.
  - (ii) Explain the working of 3-bit ripple counter and explain its working.

## SECTION-D

- Write a note on PROMs. Describe how to use address selection logic used to select a device out of a 04 devices connected.
  - (ii) Differentiate EPROM and PROM.
- 8. (i) Differentiate between static and dynamic memory.
  - (ii) Draw read and write control timing diagrams for accessing and writing to a memory location.

### 3051(2519)/EBH-1131

2

1500

www.a2zpapers.com www.a2zpapers.com ad free old Question papers gndu, ptu hp board, punjak