

Exam. Code : 105702

Subject Code : 7164

**B.Sc. (Information Technology) 2nd Semester
(Old Syllabus 2018)**

PRINCIPLES OF DIGITAL ELECTRONICS

Paper—III

Time Allowed—3 Hours]

[Maximum Marks—75

Note :— Attempt any 5 questions. All questions carry equal marks.

1. Do the following :

(i) Convert $(35.12)_{10}$ into binary

(ii) Convert ED9 into octal code.

(iii) Multiply $(121)_8$ with $(25)_8$.

(iv) $(113-67)$ using two's complement.

2. Design a Modulo-10 counter.

3. Design a half adder using NOR gates only.

4. (i) Design a binary to BCD encoder

(ii) Simplify $F = \Sigma(1,3,5,6,8)$ using Boolean algebra.

5. Explain the working of clocked RS flip-flop and JK flip flop. Also give limitations of these.

6. Write a note on EPOMs. Compare static and dynamic memory.
7. Write the steps of K-map simplification and simplify $\Sigma(1,3,4,6,8,10,12,14)$ using K-map. What is the significance of don't care terms ?
8. (i) Differentiate RAM and ROM
(ii) Explain the design and working of 4-bit shift register.