

Exam. Code : 105702

Subject Code : 1441

B.Sc. (Information Technology) 2nd Semester

(Batch 2021-24)

PRINCIPLES OF DIGITAL ELECTRONICS

Paper—I

Time Allowed—3 Hours] [Maximum Marks—75

Note :— Attempt FIVE questions in all, selecting at least ONE question from each section. The fifth question may be attempted from any section. All questions carry equal marks.

SECTION—A

1. (i) Write Gray code for 10110_2 .
(ii) Convert $(135.12)_8$ into binary.
(iii) Convert 10010010 into hexadecimal code.
(iv) Multiply $(38)_8$ with $(25)_8$.
2. Do the following :
 - (i) $(240-113)$ using 2's complement.
 - (ii) Write the excess-three codes for decimal numbers 40.

SECTION—B

3. (i) Design a full adder using NAND gates only.
(ii) Use K-map to simplify $F = \Sigma(1, 3, 4, 5, 10, 13, 15)$.
4. (i) Convert $(A + B + C)(B + C)$ into standard POS form.
(ii) Simplify $F = \Sigma(1, 3, 5, 7, 9)$ using Boolean algebra.

SECTION—C

5. (i) Explain the working of JK flip-flop.
(ii) Explain the working of serial in parallel out shift register.
6. (i) Design and explain the working of 1 to 4 demultiplexer.
(ii) Explain the working of 2-bit synchronous counter and explain its working.

SECTION—D

7. (i) Describe the selection logic used to select a device out of a 04 devices connected.
(ii) Differentiate PROM and EPROM.
8. (i) Differentiate between static and dynamic memory.
(ii) Draw read and write control timing diagrams for accessing and writing to a memory location.