

Exam. Code : 209001

Subject Code : 3750

M.Sc. Physics 1st Semester

ELECTRONICS

Paper : PHY-401

Time Allowed—3 Hours] [Maximum Marks—100

Note :— Attempt five questions in all by selecting at least one from each section. All questions carry equal marks.

SECTION—A

1. (a) Draw the structure of n-channel enhancement type MOSFET and explain its operation and characteristics. 10
- (b) Discuss the application of UJT as waveform generator using appropriate equations and waveforms. 10
2. (a) Draw two transistor equivalent circuit of SCR and discuss its operation and I-V characteristics. 10
- (b) Draw and explain typical drain characteristics for an n-channel enhancement type MOSFET and show how its transfer characteristics be obtained from drain characteristics. 10

SECTION—B

3. (a) Draw the circuit of a differential amplifier and explain its operation for differential and common mode inputs. 10
- (b) What is the need of Schmitt trigger circuit ? Draw its diagram and explain its operation. 10
4. (a) Draw the circuit of a logarithmic amplifier and obtain the expression for output voltage. Give the utility of this circuit. 10
- (b) What is an operational amplifier ? Show how it is used as inverting, non-inverting, scaling and summing amplifiers. 10

SECTION—C

5. (a) What are logic gates ? Give truth tables of all logic gates. Justify why NAND and NOR gates are called universal gates. 10
- (b) Simplify the following expression using K-map and implement the resulting reduced expression using logic gates :
- $$F(w, x, y, z) = \Sigma m(1, 4, 5, 6, 7, 9, 12). \quad 10$$
6. (a) Distinguish between encoders and decoders. Design a decimal to BCD encoder. 10

- (b) Describe the need and operation of basic parity generating and checking circuits. 10

SECTION—D

7. (a) What is a flip flop ? Give its different types. Draw the diagram of positive edge triggered SR flip flop and explain its working using suitable waveforms. 10
- (b) What are Up/Down counters ? Describe the working of Mod-8 Up/Down counter. 10
8. (a) What is the need of D/A converter ? Describe the working of ladder type D/A converter using suitable diagram and expressions. 10
- (b) What are the performance parameters of A/D converters ? Describe the working of counter type A/D convertor. 10